

Lab 8: Implement a RISC single Cycle Processor

Task 1: Using blocks from lab 7 and other glue logic, implement single cycle processor RISC which could run instructions/test file given.(you could use 32 bit reg file and 32 bit ALU from lab 7)

75 Points

Task 2: Write a program to add 5 numbers and store the result in data memory location X. (show the encoding process and machine language instruction with comments in the report). Also add screen shots of numbers in memory and result location in the report.

25 Points

Submission :

Submit single doc/pdf file with above answer and *.circ file(s) . **Due on 6th** November 2022, 11.30PM. **Submission link.**

<https://u.pcloud.com/#page=puplink&code=a2E7ZfjUqWsGprVSLK1HtgW6n0XnqJhNX>